


**NATIONAL BUSINESS AND TECHNICAL EXAMINATIONS BOARD NATIONAL TECHNICAL CERTIFICATE EXAMINATION**

**QUESTION 1**

**BASIC ELECTRICITY**


- 1(a) Explain the following terms in relation to atomic structure
- (i) Proton
  - (ii) Neutron
  - (iii) Electron
- (b) Three cells of emf 1.5 volts with an internal resistance of  $2\Omega$  each are connected in series to an external resistance of  $3\Omega$ . Calculate
- (i) total electromotive force of the battery
  - (ii) current flowing through the  $3\Omega$

**SOLUTION**

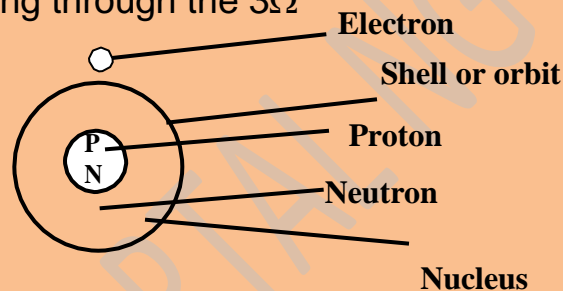

- a.i. The proton is the positively charged elementary particle that forms the nucleus of an atom. It is about 1836 times heavier than the electron. It has a stable unit charge of mass  $1.67 \times 10^{-27}$  kg. For a neutral atom the number of protons is always equal to the number of electron.
- a(ii) The neutron is also an elementary particle in an atom, having zero charge and rest mass of  $1.67492 \times 10^{-27}$  kg. It is a constituent of the atomic nucleus of an atom. Both the neutron and the proton forms the central massive part of the atom called the nucleus
- a(iii) The Electron is the negatively charged elementary particles found on the shell or orbit of the atom. It has charge of  $1.602192 \times 10^{-19}$  coulombs and a mass of  $9.10956 \times 10^{-31}$  kg. The number of electrons is equal to the number of protons in a neutral atom.

1b.

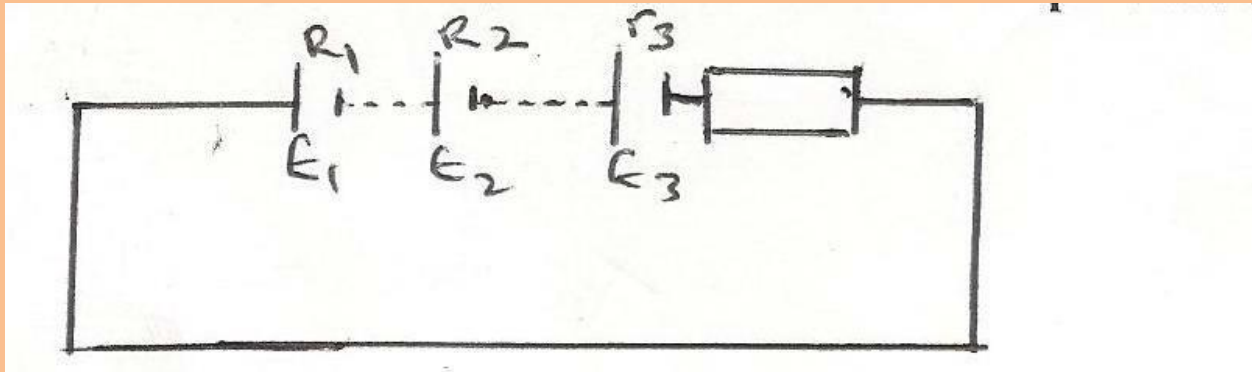

$$\begin{aligned} \text{Total internal resistance, } r_T &= r_1 + r_2 + r_3 \\ &= 2 + 2 + 2 \\ &= 6\Omega \end{aligned}$$

$$\begin{aligned} \text{(i) Total emf, } &= E_1 + E_2 + E_3 \text{ (series)} \\ &= 1.5 + 1.5 + 1.5 \\ &= \underline{4.5V} \end{aligned}$$

total resistance in the circuit is

$$\begin{aligned} R_T &= R + r_T \\ &= 3 + 6 \\ &= \underline{9\Omega} \end{aligned}$$

(ii) Current in the circuit = the current through the 3Ω resistor

$$\begin{aligned} I &= \frac{E}{R+r} \\ &= \frac{4.5}{3+6} = \frac{4.5}{9} \\ I &= \frac{4.5}{9} = 0.50A \end{aligned}$$

$$\therefore I = \underline{\quad} 0.50A$$

This is the current through the 3Ω resistor

## QUESTION 2

2. (a) Define the following and give TWO examples of each


- (i) Insulator
- (ii) Conductor

(b) An orange of mass 50g falls from rest from a height of 40m. Calculate the kinetic energy of the orange after falling a distance of 25m. (Neglect air resistance Take  $g = 10\text{m/S}^2$ ).

SOLUTION

2(a) (i) An insulator is a material that does not allow electrons to pass through it freely. It is therefore a non-conductor of heat and electricity. Examples are plastic, wood, paper, silk, wool, e.t.c.

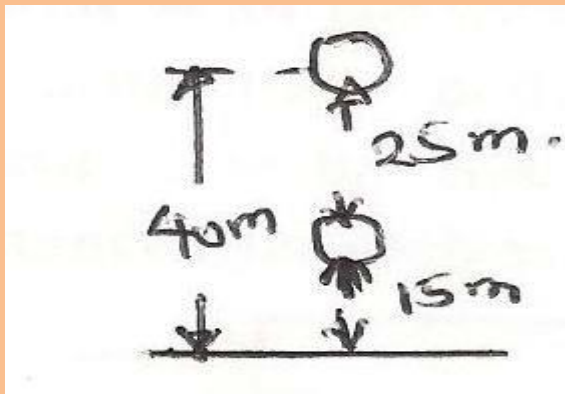(ii) A conductor is a material that allows charges to pass through it freely. It is therefore called conductor of heat and electricity. Examples are metals, the human body, the earth, electrolytes, e.tc.



2(b)

mass = 50g =  $50 \times 10^{-3}$ kg

U = 0

v = 0

g =  $10 \text{ms}^{-2}$

h = 40m

$$s = ut + \frac{1}{2}gt^2$$

$$S = 0 + \frac{1}{2}gt^2$$

$$t^2 = \frac{2s}{g}$$

$$t = \frac{\sqrt{2s}}{g} = \frac{\sqrt{2 \times 25}}{10}$$

$$= \frac{\sqrt{50}}{10}$$

$$\therefore t = 2.24\text{s}$$

$$\begin{aligned}\text{But } v &= U + gt \\ &= 0 + 10 \times 2.24 \\ &= \underline{22.4\text{ms}^{-1}}\end{aligned}$$

OR

$$\begin{aligned}V^2 &= u^2 + 2gh \\ V^2 &= 0 + 2 \times 10 \times 25 \\ V^2 &= \underline{500} \\ V &= \sqrt{500} \\ &= \underline{22.4\text{ms}^{-1}}\end{aligned}$$


$$\begin{aligned}\text{K.E.} &= \frac{1}{2}mv^2 \\ &= \frac{1}{2} \times 50 \times 10^{-3} \times (22.4)^2 \\ &= 25 \times 501.76 \times 10^{-3} \\ &= 12544 \times 10^{-3} \\ &= \underline{12.5\text{J}}\end{aligned}$$

Question3

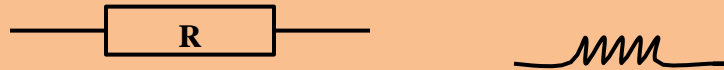3. (a) What is a Resistor? Give its symbol  
(b) List THREE types of Resistors  
(c) Three resistors of values  $15\Omega$ ,  $20\Omega$  and  $30\Omega$  are connected in series. If a voltmeter connected across the  $20\Omega$  resistor reads  $90\text{V}$ , calculate:
- total resistance of the circuit
  - current in the  $30\Omega$  resistor
  - Voltage drop in the  $15\Omega$  resistor
  - Power consumed by the circuit

SOLUTION


3(a) Resistor is an electrical component or electrical conductor which is constructed to have a precise or definite value of resistance. As an electrical component, it forms opposition to the free flow of electric current. Resistor is made with a length of resistance wire such as constantan and Nichrome. the symbol of a resistor is given as



(b) Types of Resistors

- (i) Wire-wound Resistor (Fixed Resistor)
- (ii) Moulded -carbon Resistor
- (iii) Rheostat/potentiometer/variable Resistor
- (iv) High stability resistor (carob film Resistor)

(c)

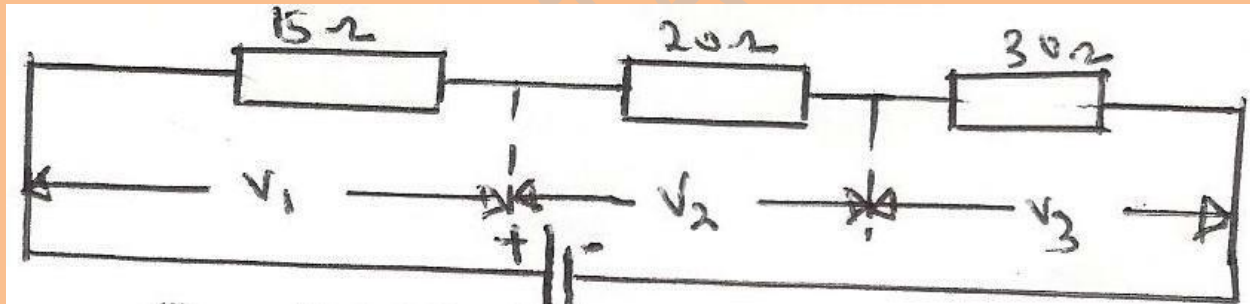

(i) Total Resistance  $R_T$

$$\begin{aligned} R_T &= R_1 + R_2 + R_3 \text{ (series)} \\ &= 15 + 20 + 30 \\ &= \underline{65\Omega} \end{aligned}$$

(ii) Current in the  $30\Omega$  resistor. The current across the three resistors  $15\Omega$ ,  $20\Omega$  and  $30\Omega$  is the same because they are in series.

Current in the  $20\Omega$  resistor of voltage drop  $90V$  is

$$I = \frac{V_2}{R_2} = \frac{90}{20} = 4.5A$$

$$I = 4.5A$$

⇒ Current in the  $30\Omega$  resistor is 4.5A

(iii) Voltage drop,  $V_1$  in the  $15\Omega$  resistor

$$V_1 = IR_1 = 4.5 \times 15$$

$$\underline{\underline{67.5V}}$$

Similarly, the voltage drop in the  $30\Omega$  resistor is

$$V_3 = IR_3 = 4.5 \times 30 = 135v$$

$$\therefore \text{Total p.d, } V_T = V_1 + V_2 + V_3$$

$$= 67.5 + 90 + 135$$

$$= \underline{\underline{292.5v}}$$

(iv) Power consumed by the circuit is P

$$P = IV \text{ or } V^2/R \text{ or } I^2R$$

$$P = IV = 4.5 \times 292.5 = 1316.25W$$

$$= V^2/R = \frac{(292.5)^2}{65} = 1316.25W$$

$$= I^2R = (4.5)^2 \times 65 = 1316.25W$$

Question 4

4. (a) Define capacitance and state its unit of measurement  
 (b) Enumerate FOUR types of capacitors  
 (c) Three capacitors of values  $5\mu f$ ,  $15\mu f$  and  $30\mu f$  are connected in series. Another capacitor of value  $50\mu f$  is connected in parallel with the series group across a 200V d.c. source. Calculate.  
 (i) total capacitance of the series group  
 (ii) total capacitance of the circuit  
 (iii) total charge stored in the capacitor  
 (iv) energy stored by the  $50\mu f$  capacitor

Solution


4a. The ability of a capacitor to store electric charges is known as capacitance. It can also be defined as the ratio of the amount of electricity (charge), Q transferred from one plate to the other, to the potential difference produced between the plates. The symbol is C and it is given as  $C = Q/V$

The unit of measurement of the capacitance is Farad F (coulomb per volt).

4(b) Types of Capacitors

- (i) Paper capacitor
- (ii) Electrolytic capacitor
- (iii) Ceramic capacitor
- (iv) Silver mica capacitor
- (v) Polyester capacitor & poly carbonate capacitor
- (vi) Tantalum capacitor
- (vii) Polystyrene capacitor

4(c)

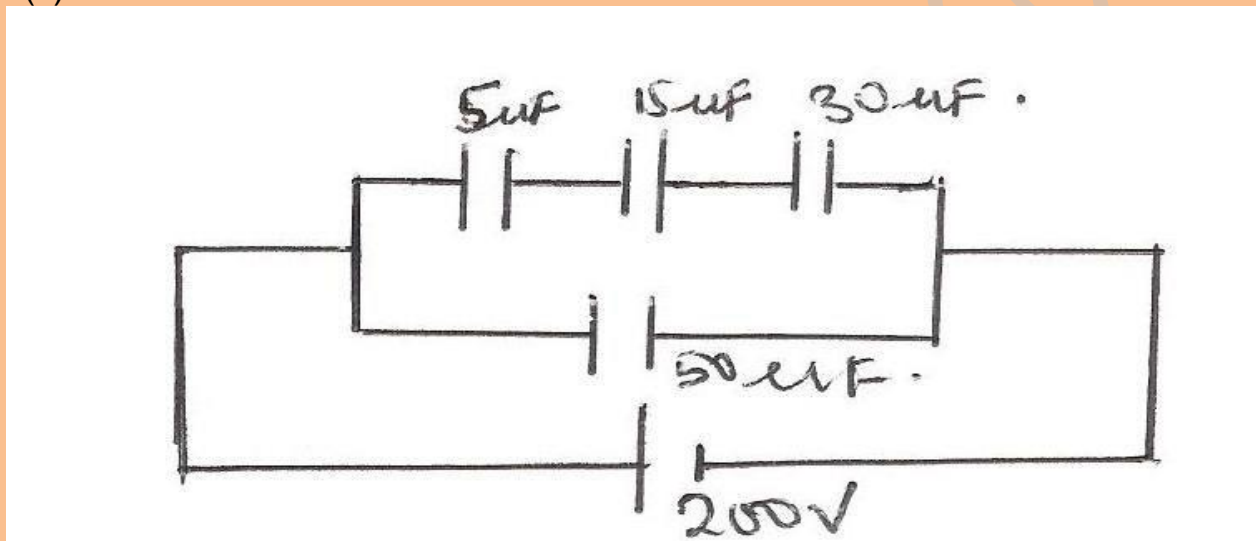

(i) Total capacitor in series group

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$= \frac{1}{6} + \frac{1}{2} + \frac{1}{3}$$

$$= \frac{9}{30}$$

$$\Rightarrow C_s = \frac{30}{9} = 3.33$$

$$\therefore C_s = \underline{3.33\mu\text{f}}$$

(ii) Total capacitance of the circuit

$$C_T = C_s + C$$

$$= 3.33 + 50$$

$$\underline{53.33\mu\text{f}}$$

(iii) Total charge stored in the capacitor

$$\begin{aligned}Q_T &= C_T V \\ &= 53.33 \times 200 \\ &= \underline{1066 \mu\text{C}} \text{ or } 1066 \times 10^{-6} \text{ or } 1.07 \times 10^{-2} \text{C}\end{aligned}$$

(iv) Energy stored by the 50 $\mu\text{f}$  capacitor.

$$\begin{aligned}W &= \frac{1}{2} C V^2 \\ &= \frac{1}{2} \times 50 \mu\text{f} \times (200)^2 \\ &= 25 \times 40000 \times 10^{-6} \text{J} \\ &= 1000 \text{ 000} \times 10^{-6} \text{J} = 1.0 \text{J}\end{aligned}$$

Question 5

5 (a) Define the following terms in relation to alternating current and state their

symbols

- (i) inductive reactance
- (ii) impedance

(b) A 200 $\mu\text{f}$  capacitor is connected in series with a 60 $\Omega$  resistor. The combinations is connected to a 200V, 50Hz supply. Calculate:

- (i) capacitive reactance of the capacitor
- (ii) inpendance of the circuit
- (iii) current
- (iv) power factor

Solution


5a(i) Inductive Reactance is the opposition to alternating current due to the presence of an inductor in the circuit. It is given as  $X_L$  and can be obtained from the relationship that,  $X_L = 2\pi fL$ . The symbol is  $X_L$  and its unit is ohms.

a(ii) Impedance is the effective or total opposition to alternating current due to the presence of an inductance coil (an inductor), the capacitor and a resistor in an A.C. circuit.

The impedance is represented with a symbol  $Z$  and its unit is ohms.



5(b)

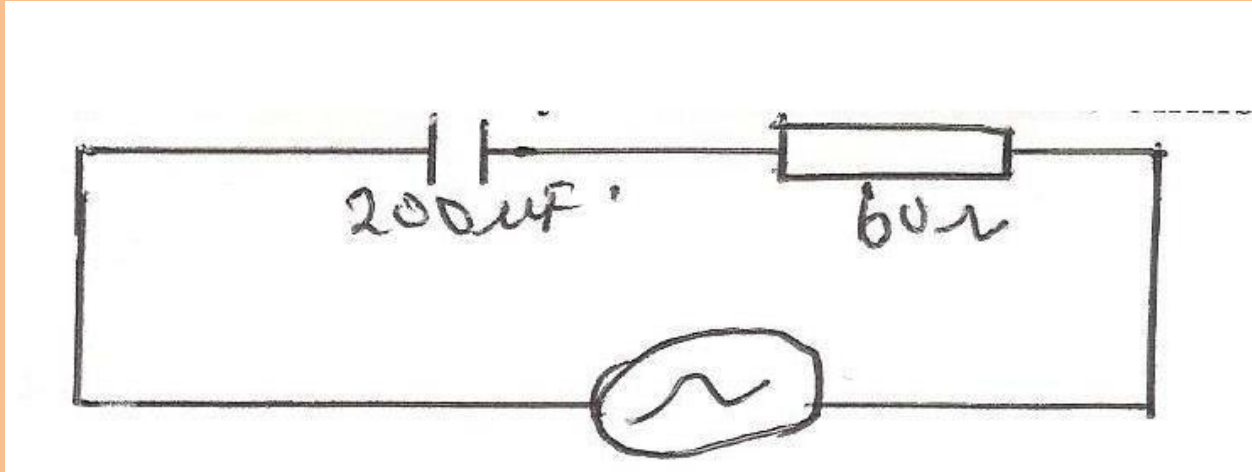

(i) Capacitive reactance of the capacitor

$$\begin{aligned} X_c &= \frac{1}{2\pi f c} \\ &= \frac{1 \times 10^6}{2 \times 3.142 \times 50 \times 200} \\ &= \frac{10^6}{62840} \\ &= \underline{15.91\Omega} \end{aligned}$$

(ii) Impedance of the circuit

$$\begin{aligned} Z &= \sqrt{R^2 + (X_c)^2} \\ &= \sqrt{60^2 + (15.91)^2} \\ &= \sqrt{3600 + 253.13} \\ &= \sqrt{3853.13} \\ &= \underline{62.1\Omega} \end{aligned}$$

(iii) Current, I

$$I = \frac{V}{Z} = \frac{200}{62.1} = 3.22$$

$$\therefore I = \underline{3.22A}$$

(iv) Power factor


$$\begin{aligned} \text{pf} &= \frac{R}{Z} = \frac{60}{62.1} \\ &= \underline{0.97 \text{ leading.}} \end{aligned}$$


Question 6

Draw the following symbols to British Standards (BS):

(i)  Energy Meter

(ii)  Voltmeter

(iii)  Plug

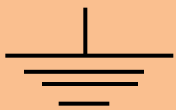
(iv)  Earth


(v)  Transformer or

(vi)  Variable Inductance

(vii)  Diode

(viii)  Variable Resistor

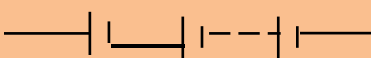(ix)  Battery

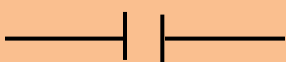(x)  Capacitor

GET MORE ON SCHOOL PORTAL NG  
(<https://schoolportalng.com>)

---

SCHOOL PORTAL NG . COM